

GOVERNMENT POLYTECHNIC, NAYAGARH

**DIGITAL ELECTRONIC
&
MICROPROCESSOR
LABORATORY MANUAL**

ER. JADUNATH MURMU
Sr. Lecture in Electronics

ER. KUMAR AVISEK
Lab. Asst. (A.E. & I)

**DEPARTMENT OF ELECTRICAL
ENGINEERING**



LABORATORY MANUAL
Digital Electronics & Microprocessor Lab
(5th Semester)

Govt. Polytechnic, Nayagarh

At - Ghasadeipur, Po - Nandighore
Pin - 752081

Approved by : Jadunath Murmu
Prepared By : Er. Kumar Avisek
Lab. Asst. (A. E. & I.)



GOVT. POLYTECHNIC NAYAGARH -752081
Department of Skill Development & Technical Education
Govt. of Odisha ,Bhubaneswar

The Vision of the Institute

To emerge as a leading Technical Institution by imparting knowledge in field of Engineering and Technology to its pass outs to make them Industry employable and self enterprising so as to serve society in order to achieve harmonious relation between Human habitant and Nature in an Eco friendly environment

The Mission of the Institute:

- To deliver knowledge at par with cutting edge technology& promote academic growth
- To facilitate a creative and independent learning environment
- To develop a co-relation between academia, industry and society through various consultancy and testing constructional materials.
- To transform individuals by inculcating values, ethics and leadership qualities
- To establish an atmosphere where management principles and techniques will nurture in fulfilment of institutional aims and objectives



GOVT. POLYTECHNIC NAYAGARH -752081
Department of Skill Development & Technical Education
Govt. of Odisha, Bhubaneswar

PROGRAM EDUCATIONAL OBJECTIVE

PEO 1: Students are able to apply knowledge of basic science, computer fundamentals and basic principles of electrical engineering.

PEO 2: Students are able to enhance their analytical and problem solving ability using theoretical and practical knowledge to solve real time problem in electrical domain.

PEO 3: Students become adaptable to work in multi-disciplinary environment through continuous development of technical skills, professional efficiency.

PROGRAM SPECIFIC OUTCOME

PSO1: Ability to apply domain knowledge in testing and maintenance of electrical machine and equipment

PSO2: Ability to prepare design and estimate of various electrical installations.

PSO3: Contribute for the generation and utilization of green energy to meet the increasing demand of the society



GOVT. POLYTECHNIC NAYAGARH -752081
Department of Skill Development & Technical Education
Govt. of Odisha, Bhubaneswar

THE VISION OF THE DEPARTMENT

Empowering Electrical Professionals with strong ethical values and sound technical knowledge and unique set of skills which will enable to a rousing start to fulfill the future demands and needs of the industry and society to achieve sustainable development.

THE MISSION OF THE DEPARTMENT

- To align the teaching learning process and to provide basic foundation for the students to adapt to the changing industrial needs.
- To provide an atmosphere of Independent learning where they can be nurtured with qualities like leadership, responsibility and optimistic.
- To update the curriculum and learning materials in consultation with industry professionals to make students industry ready.
- To enrich with the latest developments through seminars, guest lectures, workshop and industry visits through interaction with industry professionals.
- To develop professional competency and technical expertise individually and through team effort thereby exhibit leadership in industry.

DIGITAL ELECTRONICS & MICROPROCESSOR LAB

CO1. Familiar with use of Digital ICs.

CO2. Understand the simple Digital circuit

CO3. Understand the counter and register

CO4. write and execute Assembly Language program

CO5. Application of 8085 using interfacing

CO and PO Mapping Matrix										
CO	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PSO1	PSO2	PSO3
Familiar with use of Digital ICs.	3	1	1	-	2	-	-	2	-	-
Understand the simple Digital circuit	3	1	2	2	1	-	-	-	-	-
Understand the counter and register	3	1	1	2	1	-	-	2	-	-
write and execute Assembly Language program	3	1	2	2	2	-	2	-	-	-
Application of 8085 using interfacing	3	-	2	3	3	-	-	-	-	-
AVERAGE	3	0.8	1.6	1.8	1.8	-	0.4	0.8	-	-


TABLE OF CONTENTS

Sl. No.	Name of the Experiment	Pages
1.	Verify truth tables of AND, OR, NOT, NOR, NAND, XOR, XNOR gates.	8
2.	Implement various gates by using universal properties of NAND & NOR gates and verify truth table.	11
3.	Implement half adder and Full adder using logic gates.	15
4.	Implement half subtractor and Full subtractor using logic gates.	18
5.	Implement a 4-bit Binary to Gray code converter.	22
6.	Implement a Single bit digital comparator.	27
7.	Study Multiplexer and demultiplexer.	29
8.	Study of flip-flops. i) S-R flip flop ii) J-K flip flop iii) flip flop iv) T flip flop	36
9.	Realize a 4-bit asynchronous UP/DOWN counter with a control for up/down counting.	42
10.	Realize a 4-bit synchronous UP/DOWN counter with a control for up/down counting.	45
11.	Study shift registers.	52


TABLE OF CONTENTS

Sl. No.	Name of the Experiment	Pages
12.	1'S Complement 2's Complement	56
13.	Addition of 8- bit number.	57
14.	Subtraction of 8-bit number resulting 8/16 bit number	58
15.	Find the largest in an Array	59
16.	Block Transfer.	60
17.	Traffic light control using 8255	61
18.	Generation of square wave using 8255	67


Inverter Gate (NOT Gate) 7404LS

 


2-Input AND Gate 7408LS

 


2-Input OR Gate 7432LS

 


2-Input NAND Gate 7400LS

 


2-Input NOR Gate 7402LS

 

2-Input XNOR Gate 74266LS

 

2-Input XOR Gate 7486LS

 

Experiment No:1

Date: __/__/____

Aim: - To Verify truth tables of AND, OR, NOT, NOR, NAND, XOR, XNOR gates.


Apparatus Required: -

1. All the basic gates mention in the fig.
2. IC Trainer Kit

Procedure: -


1. Place the IC on IC Trainer Kit.
2. Connect V_{CC} and ground to respective pins of IC Trainer Kit.
3. Connect the inputs to the input switches provided in the IC Trainer Kit.
4. Connect the outputs to the switches of O/P LEDs,
5. Apply various combinations of inputs according to the truth table and observe condition of LEDs.
6. Disconnect output from the LEDs and note down the corresponding multimeter voltage readings for various combinations of inputs.

Inverter Gate (NOT Gate) 7404LS

 


A	O/P
0	1
1	0

2-Input AND Gate 7408LS

 


A	B	O/P
0	0	0
0	1	0
1	0	0
1	1	1

2-Input OR Gate 7432LS

 


A	B	O/P
0	0	0
0	1	1
1	0	1
1	1	1

2-Input NAND Gate 7400LS

 


A	B	O/P
0	0	1
0	1	1
1	0	1
1	1	0

2-Input NOR Gate 7402LS

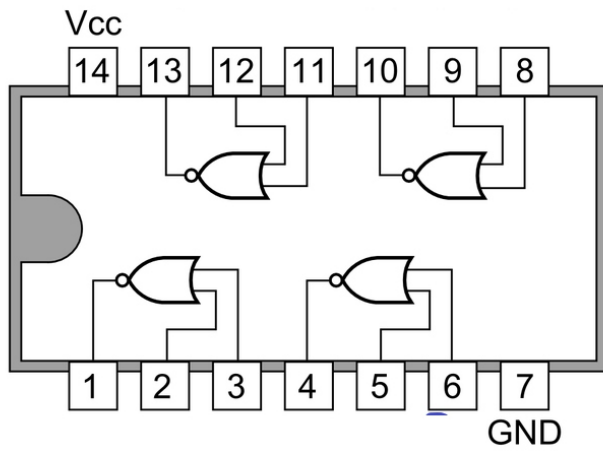


A	B	O/P
0	0	1
0	1	0
1	0	0
1	1	0

2-Input XOR Gate 7486LS

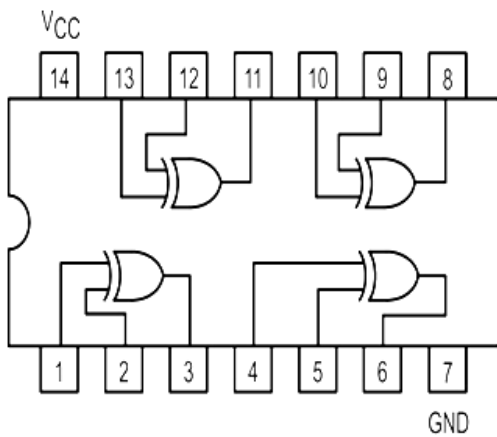

A	B	O/P
0	0	0
0	1	1
1	0	1
1	1	0

2-Input XNOR Gate 74266LS

 

A	B	O/P
0	0	1
0	1	0
1	0	0
1	1	1

Conclusion:-
Truth table of logic gates are verified.

Experiment No:2

Date: __/__/____

Aim: - Implementation of various gates by using universal properties of NAND & NOR gates and Verify truth table.

APPARATUS REQUIRED

1. Digital IC trainer kit
2. IC 7400 (NAND gate)
3. IC 7402(NOR gate)


THEORY:

NAND OR NOR gates are sufficient for the realization of any logic expression. because of this reason, NAND and NOR gates are known as UNIVERSAL gates.

1. For NAND gate as universal gate


PROCEDURE:

 1. Make the connections as per the logic diagram.
2. Connect +5v to pin 14 & ground to pin 7 of IC 7400
3. Apply diff combinations of inputs to the i/p terminals.
4. Note o/p for NAND as universal gate.
5. Verify the truth table.




(a) NOT Logic Operation

A	\bar{A}
0	1
1	0

 


(b) AND Logic Operation

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

 


(c) OR Logic Operation

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

 


NOR Logic operation

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

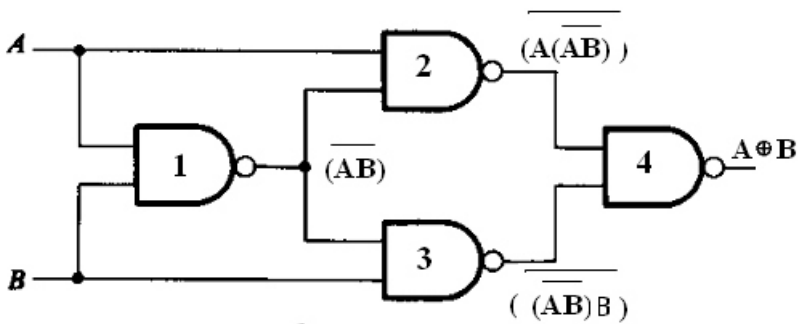

XOR Logic operation

A	B	A ⊕ B
0	0	0
0	1	1
1	0	1
1	1	0

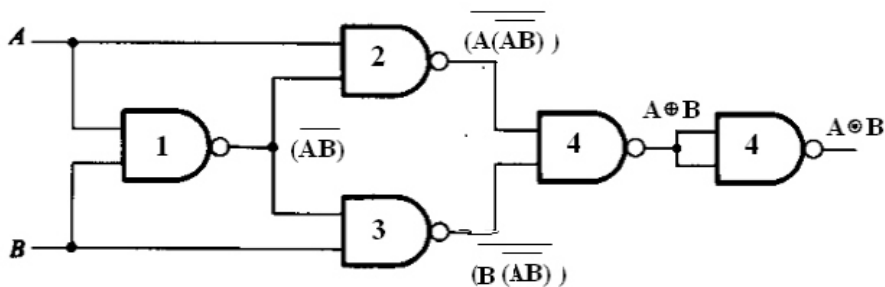

XNOR Logic operation

A	B	A ⊕ B
0	0	1
0	1	0
1	0	0
1	1	1

2. For NOR gate as universal gate

PROCEDURE:

1. Make the connections as per the logic diagram.
2. Connect +5v to pin 14 & ground to pin 7 of IC 7402
3. Apply diff combinations of inputs to the i/p terminals.
4. Note o/p for NAND as universal gate.
5. Verify the truth table




NOT Logic operation

A	\bar{A}
0	1
1	0




OR Logic operation

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

 


AND Logic operation

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

 


NAND Logic operation

A	B	AB
0	0	1
0	1	1
1	0	1
1	1	0

 

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XOR Logic operation

 

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

Conclusion:-

We have constructed and verified truth table of all gates using universal gates NAND and NOR gate.

Experiment No:3

Date: __/__/____

Aim: - Implementation of half adder and Full adder using logic gates.

APPARATUS REQUIRED

- 1.IC 7486, IC 7432, IC 7408, IC 7400.
- 2.Digital trainer kit.

THEORY:

Half-Adder: A combinational logic circuit that performs the addition of two data bits, A and B, is called a half-adder. Addition will result in two output bits; one of which is the sum bit, S, and the other is the carry bit, C. The Boolean functions describing the half-adder are:


$$S = A \oplus B \qquad C = A B$$

Full-Adder: The half-adder does not take the carry bit from its previous stage into account. This carry bit from its previous stage is called carry-in bit. A combinational logic circuit that adds two data bits, A and B, and a carry-in bit, C_{in} , is called a full-adder. The Boolean functions describing the full-adder are:


$$S = (x \oplus y) \oplus C_{in} \qquad C = xy + C_{in} (x \oplus y)$$

Procedure: -


1. Verify the gates.
2. Make the connections as per the circuit diagram.
3. Switch on V_{CC} and apply various combinations of input according to the truth table.
4. Note down the output readings for half and full adder sum and the carry bit for different combinations of inputs.

 Half Adder using basic gates:-


Full Adder using basic gates:-

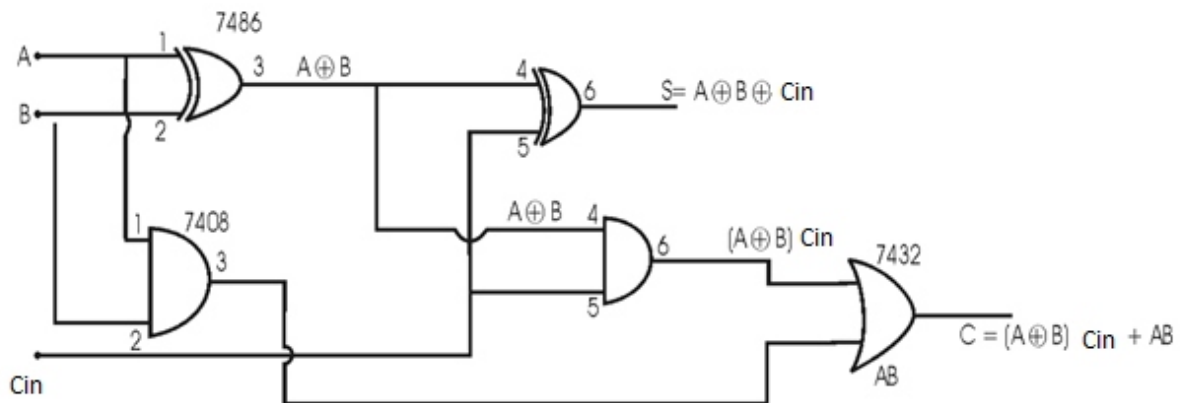

Half Adder using NAND gates only:-

 


Full Adder using NAND gates only:-

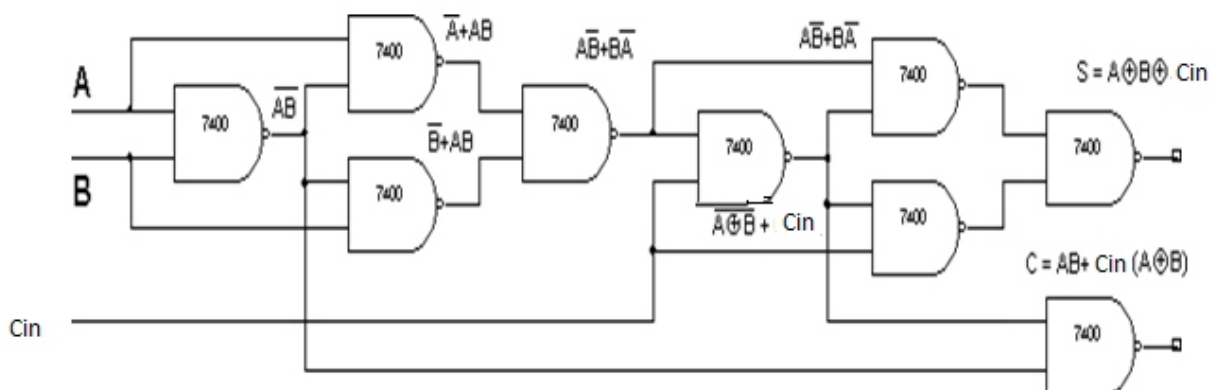


K-map for half adder

Half adder			
A	B	S	C
0	0		
0	1		
1	0		
1	1		

For S:

 

For C:

 


K Maps


K-map for full adder

Full Adder				
A	B	C _{in}	S	C
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

For S:

 

For C_{in}:

 

Conclusion: -

Half adder and full adder are constructed and their truth tables are verified.

Experiment No:4

Date: __/__/__

Aim: - Implementation of half subtractor and Full subtractor using logic gates.

APPARATUS REQUIRED

- 1.IC 7486, IC 7432, IC 7408,IC7404, IC7400.
- 2.Digital trainer kit.

THEORY:

Half Subtractor: Subtracting a single-bit binary value B from another A (i.e. A -B) produces a difference bit D and a borrow out bit B-out. This operation is called half subtraction and the circuit to realize it is called a half subtractor. The Boolean functions describing the halfSubtractor are:

$$D = A \oplus B$$

$$B_r = \bar{A} B$$

Full Subtractor: Subtracting two single-bit binary values, B, Cin from a single-bit value A produces a difference bit D and a borrow out Br bit. This is called full subtraction. The Boolean functions describing the full-subtractor are:


$$D = (x \oplus y) \oplus B_{in}$$

$$B_r = \bar{A}B + \bar{A} (B_{in}) + B (B_{in})$$


Procedure: -

 1. Verify the gates.
2. Make the connections as per the circuit diagram.
3. Switch on V_{CC} and apply various combinations of input according to the truth table.
4. Note down the output readings for half and full subtractor difference and borrow bit for different combinations of inputs.


Using X – OR and Basic Gates (a) Half Subtractor




Full Subtractor

 

Using only NAND gate (a) Half subtractor

 


(b) Full Subtractor

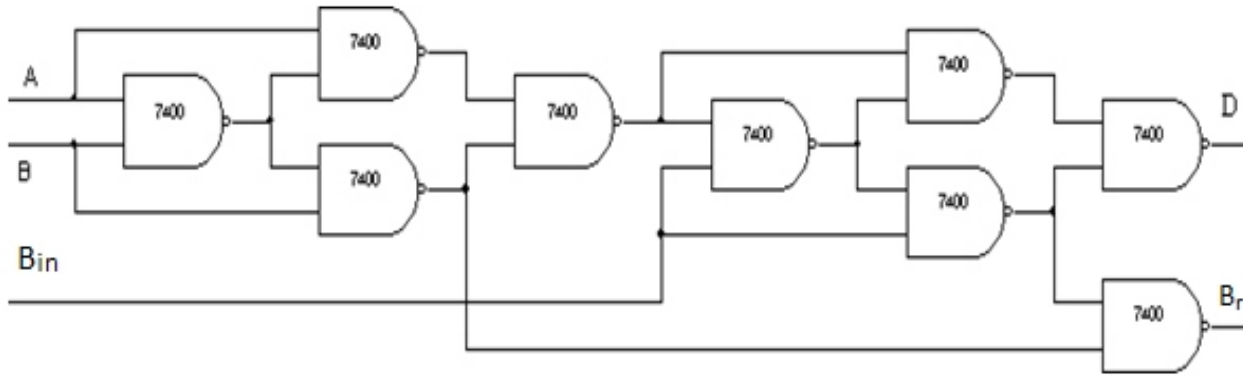


For D:

Half Subtractor			
A	B	D	B _r
0	0		
0	1		
1	0		
1	1		

 

$$D = A \oplus B$$

For B_r:

 


$$B_r = \overline{A} \cdot B$$


K Maps

Full Subtractor				
A	B	B _{in}	D	B _r
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

For D:

 

For B_r

 

Conclusion: -

Half subtractor and full subtractor are constructed and their truth tables are verified.

Experiment No:5

Date: __/__/__

Aim: - Implementation of a 4-bit Binary to Gray code converter.**APPARATUS REQUIRED**

1. IC 7486
2. Digital trainer kit

THEORY:

Gray Code is one of the most important codes. It is a non-weighted code which belongs to a class of codes called minimum change codes.

In this codes while traversing from one step to another step, only one bit in the code group changes.

The input variable are designated as B3, B2, B1, B0 and the output variables are designated as G3, G2, G1, G0.

Procedure: -

1. The circuit connections are made as shown in fig.
2. Pin (14) is connected to +Vcc and Pin (7) to ground.
3. In the case of binary to gray conversion, the inputs B0, B1, B2 and B3 are given at respective pins and outputs G0, G1, G2, G3 are taken for all the 16 combinations of the input.
4. The values of the outputs are tabulated.

TRUTH TABLE:

Binary Input				Gray code output			
B3	B2	B1	B0	G3	G2	G1	G0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1

0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

K-Map for G_3 :

		B1B0			
		00	01	11	10
B3B2	00				
	01				
	11	1	1	1	1
	10	1	1	1	1

$$G_3 = B_3$$

K-Map for G_2 :

		B1B0			
		00	01	11	10
B3B2	00				
	01	1	1	1	1
	11				
	10	1	1	1	1

$$G_2 = B_3 \oplus B_2$$

K-Map for G_1 :


		B1B0			
		00	01	11	10
B3B2	00			1	1
	01	1	1		
	11	1	1		
	10			1	1

$$G_1 = B_1 \oplus B_2$$

K-Map for G_0 :

		B1B0			
		00	01	11	10
B3B2	00		1		1
	01		1		1
	11		1		1
	10		1		1

$$G_0 = B_1 \oplus B_0$$

 LOGIC DIAGRAM**Conclusion: -**

4-bit Binary to Gray code converter is constructed and their truth tables are verified.

Experiment No:6

Date: __/__/__

Aim: - Implementation of a Single bit digital comparator.**APPARATUS REQUIRED**

1. IC 7404, IC 7408, IC 74266
2. Digital trainer kit

THEORY:

Magnitude Comparator is a logical circuit, which compares two signals A and B and generates three logical outputs, whether $A > B$, $A = B$, or $A < B$.

Procedure: -

1. The circuit connections are made as shown in fig.
2. Pin (14) is connected to +Vcc and Pin (7) to ground.
3. The inputs A, B are given at respective pins and outputs $A > B$, $A = B$, or $A < B$ are connected to the output LED.
4. The values of the outputs are tabulated.


TRUTH TABLE

INPUTS		OUTPUTS		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

$$A > B = \overline{A} B$$

$$A < B = \overline{A} B$$

$$A = B = \overline{A} \overline{B} + AB$$

 LOGIC DIAGRAM**Conclusion: -**

A Single bit digital comparator is constructed and it's truth tables are verified.

EXPERIMENT NO: -7**AIM: -**

To study Multiplexer and Demultiplexer.

APPARATUS REQUIRED: -

SL NO.	COMPONENT	SPECIFICATION	QUANTITY
1	4x1 MULTIPLEXER	IC 74153	1
2	1x4 DEMULTIPLEXER	IC 74156	1
3	BREAD BOARD	-	1
4	RESISTOR	220Ω	1
5	BATTERY	9V	1
6	LED	-	1
7	CONNECTING WIRE	-	AS PER REQUIREMENT

THEORY : -**MULTIPLEXER :**


Multiplexer generally means many into one. A multiplexer is a circuit with many inputs but only one output. By applying control signals we can steer any input to the output. The circuit has n input signals, control signal (m) & one output signal, where $2^m = n$. One of the popular multiplexers is the 16 to 1 multiplexer, which has 16 input bits, 4 control bits & 1 output bit.

4x1 Multiplexer

The 4x1 Multiplexer has four input lines, I_1 , I_2 and I_3 and one output line Y . The selection of a particular input is controlled by a set of selection lines S_1 and S_0 .

TRUTH TABLE


Selection line		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

$$Y = I_0 S_1' S_0' + I_1 S_1' S_0 + I_2 S_1 S_0' + I_3 S_1 S_0$$

CIRCUIT DIAGRAM OF 4X1 MUX USING LOGIC GATES

PIN DIAGRAM OF IC 74153

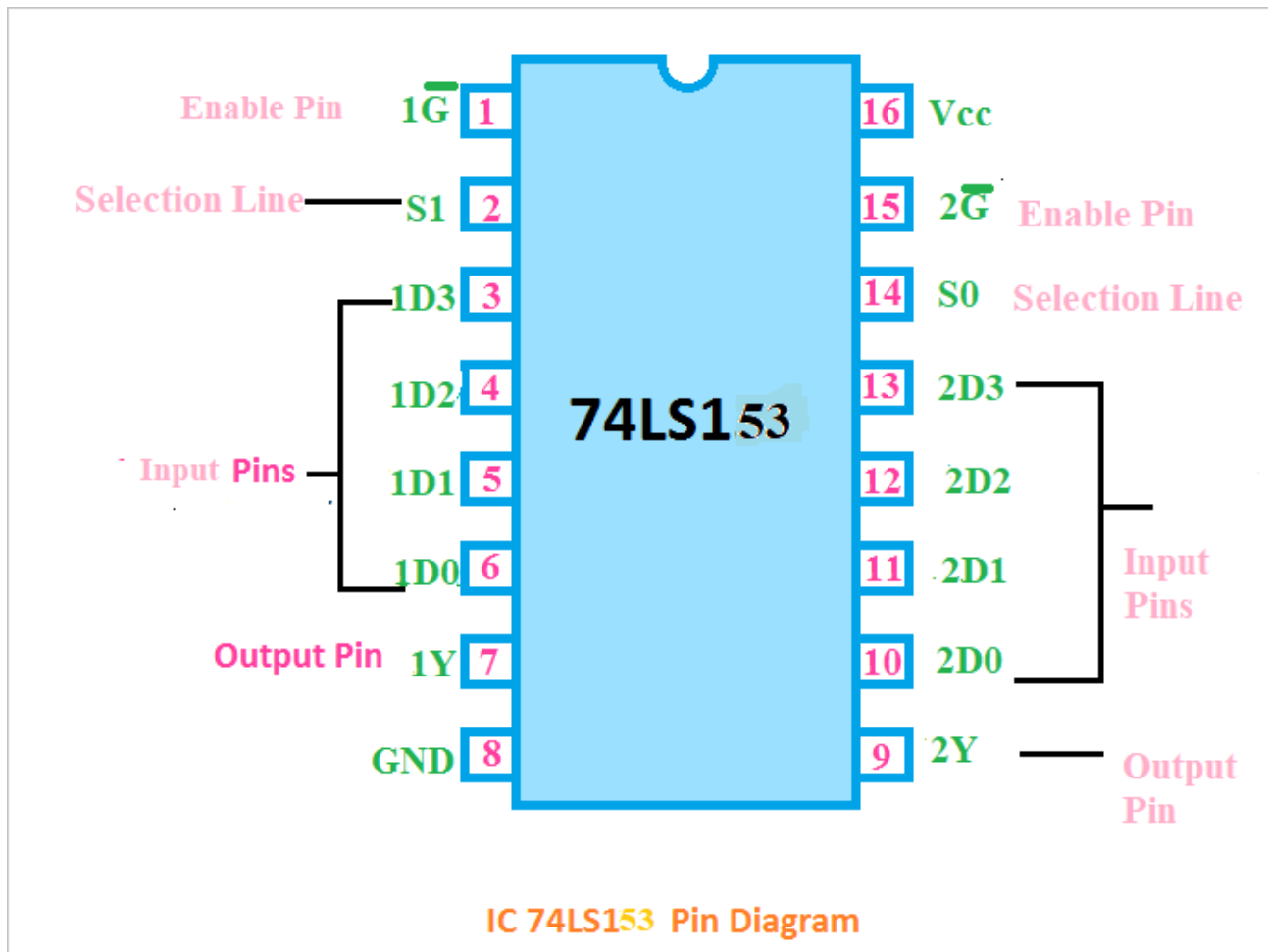

IC 74153 Truth Table

The truth table of IC 74153 is given below

Select Inputs		Inputs (a or b)					Output
A	B	a	b	c	d	e	Z
X	X	H	X	X	X	X	L
L	L	L	L	X	X	X	L
L	L	L	H	X	X	X	H
H	L	L	X	L	X	X	L
H	L	L	X	H	X	X	H
L	H	L	X	X	L	X	L
L	H	L	X	X	H	X	H
H	H	L	X	X	X	L	L
H	H	L	X	X	X	H	H

H = High voltage

L = Low voltage

X = Don't care

DEMULTIPLEXER:


Demultiplexer means generally one into many. A demultiplexer is a logic circuit with one input and many outputs. By applying control signals, we can steer the input signal to one of the output lines. The circuit has one input signal, m control signals and n output signals, where $n = 2^m$. It functions as an electronic switch to route an incoming data signal to one of several outputs.

1x4 Demultiplexer


The 1x4 Demultiplexer has one input I and four outputs Y_0, Y_1, Y_2 and Y_3 .

TRUTH TABLE

Input I	Selection line		Output			
	S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	1
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	1	0	0	0

 **CIRCUIT DIAGRAM OF 1 x 4 DEMUX**

PIN DIAGRAM OF IC 74156

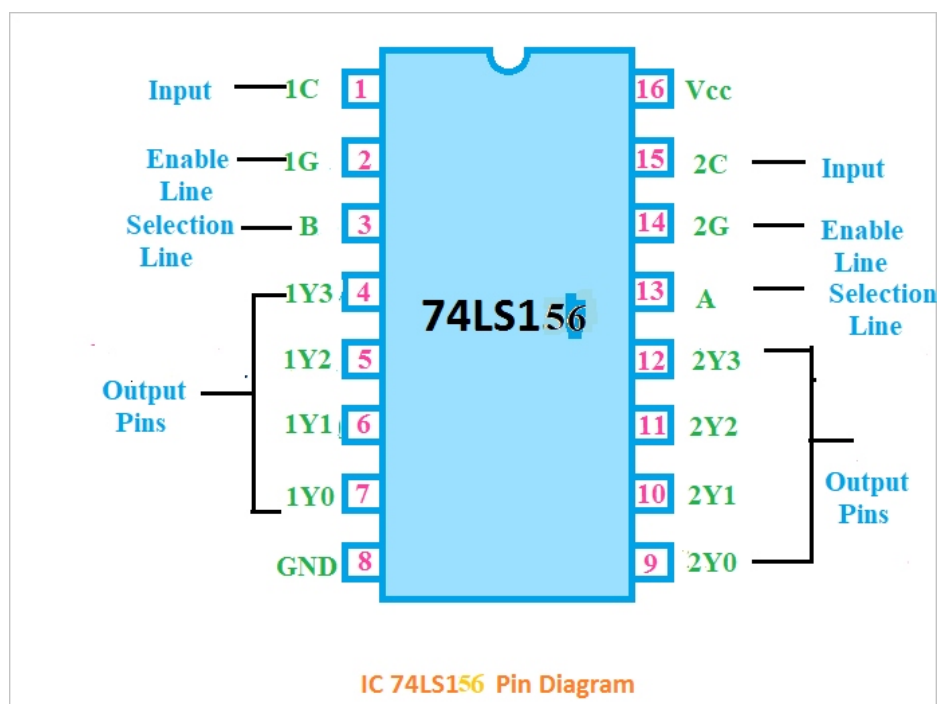

PROCEDURE: -

1. Connect the circuit as shown in figure.
2. Apply V_{CC} & ground signal to the IC.
3. Observe the input & output according to the truth table.

PRECAUTIONS: -

1. Make the connections according to the IC pin diagram.
2. The connections should be tight.
3. The V_{CC} and ground should be applied carefully at the specified pin only.

OBSERVATION: - [L=logic0, H=logic1]

4x1 Multiplexer

Input line				Selectionline		Output
I ₀	I ₁	I ₂	I ₃	S ₁	S ₀	Y
H	L	L	H	L	L	
L	L	H	H	L	H	
H	H	L	L	H	L	
L	H	L	H	H	H	

1x4 Demultiplexer

Input	Selectionline		Output			
I	S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
H	L	L				
H	L	H				
H	H	L				
H	H	H				

RESULT: - Hence, the truth table of 4x1 Multiplexer and 1x4 Demultiplexer are verified and found ok.

Experiment No : 8**AIM:**

To verify the characteristic table of RS, D, JK, and T Flip flops.

APPARATUS REQUIRED:

S.No	Name of the Apparatus	Range	Quantity
1.	Digital IC trainer kit		1
2.	NOR gate	IC 7402	
3.	NOT gate	IC 7404	
4.	AND gate (three input)	IC 7411	
5.	NAND gate	IC 7400	
6.	Connecting wires		As required

THEORY:

A Flip Flop is a sequential device that samples its input signals and changes its output states only at times determined by clocking signals. Flip Flops may vary in the number of inputs they possess and the manner in which the inputs affect the binary states.

RS FLIP FLOP:

The clocked RS flip flop consists of NAND gates and the output changes its state with respect to the input on application of clock pulse. When the clock pulse is high the S and R inputs reach the second level NAND gates in their complementary form. The Flip Flop is reset when the R input is high and S input is low. The Flip Flop is set when the S input is high and R input is low. When both the inputs are high the output is in an indeterminate state.

D FLIP FLOP:

To eliminate the undesirable condition of indeterminate state in the SR Flip Flop where both inputs are high at the same time, in the D Flip Flop the inputs are never made equal at the same time. This is obtained by making the two inputs complements of each other.

JK FLIP FLOP:


The indeterminate state in the SR Flip Flop is defined in the JK Flip Flop. JK inputs behave like S and R inputs to set and reset the Flip Flop. The output Q is ANDed with K input and the clock pulse, similarly the output Q' is ANDed with J input and the Clock pulse. When the clock pulse is zero both the AND gates are disabled and the Q and Q' output retain their previous values. When the clock pulse is high, the J and K inputs reach the NOR gates. When both the inputs are high the output toggles continuously. This is called Race around condition and this must be avoided.

T FLIP FLOP:


This is a modification of JK Flip Flop, obtained by connecting both inputs J and K input together. T Flip Flop is also called Toggle Flip Flop.

RS FLIP FLOP

LOGIC SYMBOL :


 


CIRCUIT DIAGRAM :

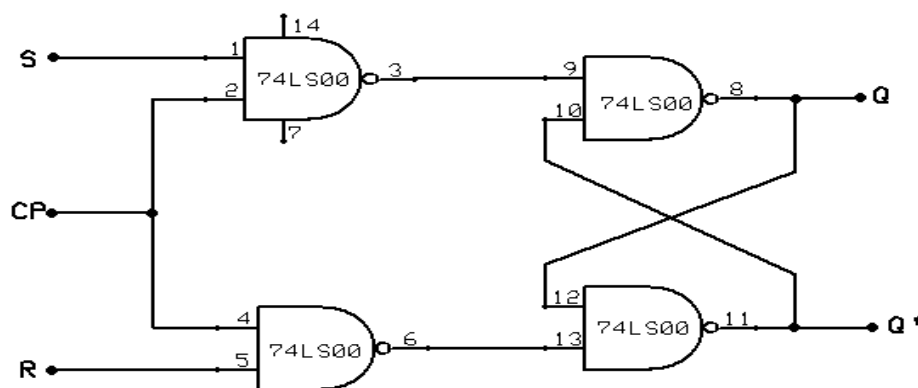



CHARACTERISTIC TABLE:

CLOCK PULSE	INPUT		PRESENT STATE (Q)	NEXT STATE (Q+1)	STATUS
	S	R			
1	0	0	0	0	
2	0	0	1	1	
3	0	1	0	0	
4	0	1	1	0	
5	1	0	0	1	
6	1	0	1	1	
7	1	1	0	X	
8	1	1	1	X	

  D FLIP FLOP**LOGIC SYMBOL:****CIRCUIT DIAGRAM:**


CHARACTERISTIC TABLE:


CLOCK PULSE	INPUT D	PRESENT STATE (Q)	NEXT STATE(Q+1)	STATUS
1	0	0	0	
2	0	1	0	
3	1	0	1	
4	1	1	1	

 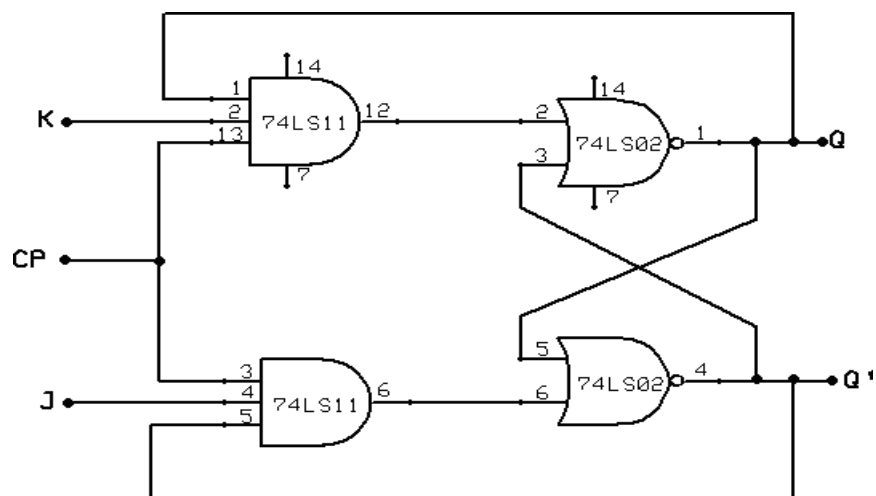JK FLIP FLOP**LOGIC SYMBOL:****CIRCUIT DIAGRAM :**

CHARACTERISTIC TABLE:

CLOCK PULSE	INPUT		PRESENT STATE (Q)	NEXT STATE(Q+1)	STATUS
	J	K			
1	0	0	0	0	
2	0	0	1	1	
3	0	1	0	0	
4	0	1	1	0	
5	1	0	0	1	
6	1	0	1	1	
7	1	1	0	1	
8	1	1	1	0	

 T FLIPFLOP**LOGIC SYMBOL:**

 CIRCUIT DIAGRAM:**CHARACTERISTIC TABLE:**

CLOCK PULSE	T	INPUT	PRESENT STATE (Q)	NEXT STATE (Q+1)	STATUS
1		0	0	0	
2		0	1	0	
3		1	0	1	
4		1	1	0	

PROCEDURE:

1. Connections are given as per the circuit diagrams.
2. For all the ICs 7th pin is grounded and 14th pin is given +5V supply.
3. Apply the inputs and observe the status of all the flip flops.

RESULT : The Characteristic tables of RS, D, JK, T flip flops were verified.

Experiment No : 9

AIM :

Realize a 4-bit asynchronous UP/Down counter with a control for up/down counting .

APPARATUS REQUIRED :

Sl. No.	COMPONENT	SPECIFICATION	QTY
1.	JK FLIP FLOP	IC 7473	2
2.	IC TRAINER KIT	-	-
3.	PATCH CORDS	-	30

THEORY:


UP-COUNTER :

Asynchronous counters are the circuit that used to count the binary numbers in prescribed sequence. In asynchronous counter the flip-flops are not triggered with common clock pulse. Except the first (least significant) flip-flop others are triggered by the output of previous flip-flop while the first one is triggered by the clock pulse. Hence asynchronous counter is also called as ripple counter. When inputs set into logic high the JK flip-flops are continuously present in the toggle condition which complements the output continuously. This cause to prevent the circuit from triggering of two adjacent flip-flops simultaneously.

DOWN-COUNTER :

Asynchronous down counter performs the reverse operation of up-counter which counts the binary number by decreasing one when the flip-flops are activated by the clock pulse. First flip-flop triggered by clock pulse the remaining flip-flops are triggered by the inverted output of previous flip-flop. It is an only difference from up-counter.

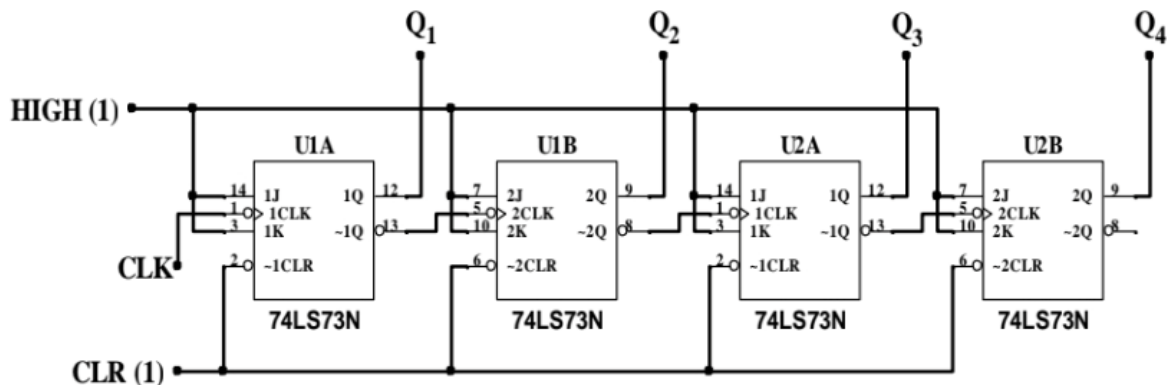
LOGIC DIAGRAM OF 4-BIT ASCHNCRONOUS (RIPPLE) DOWN-COUNTER:



TRUTH TABLE:

INPUT	OUTPUTS			
	Q ₄	Q ₃	Q ₂	Q ₁
0	1	1	1	1
1	1	1	1	0
2	1	1	0	1
3	1	1	0	0
4	1	0	1	1
5	1	0	1	0
6	1	0	0	1
7	1	0	0	0
8	0	1	1	1
9	0	1	1	0
10	0	1	0	1
11	0	1	0	0
12	0	0	1	1
13	0	0	1	0
14	0	0	0	1
15	0	0	0	0

PIN DIAGRAM OF IC 7473

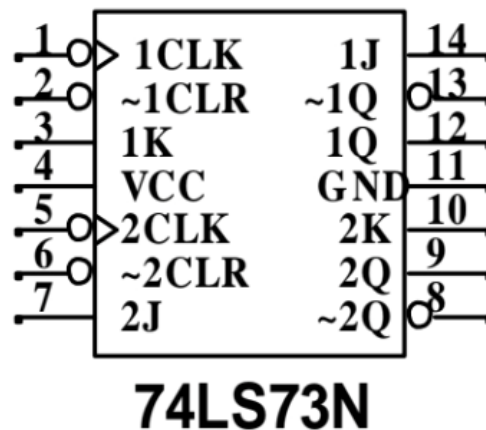

74LS73N

PROCEDURE :

1. Connections are given as per the logic diagram.
2. Apply the clock pulse and verify the truth table.

RESULT :

Experiment No : 10

AIM :

Realize a 4-bit synchronous UP/Down counter with a control for up/down counting .

APPARATUS REQUIRED :

Sl. No.	COMPONENT	SPECIFICATION	QTY
1.	JK FLIP FLOP	IC 7473	2
2.	IC TRAINER KIT	-	-
3.	PATCH CORDS	-	30

THEORY:

SYNCHRONOUS UP/DOWN COUNTER :


Up/Down counter is a circuit which perform the logic count either up or down by increasing or decreasing a number by 1. Synchronous Up/Down counter is a circuit which executes the counting operation either up or down with a commonly clocked flip-flops. In a counter the progress of Up and Down counting operations are selected by the control signal. After selecting the counting operation by enforcing the clock pulses to the flip-flops desired counting operation is executed. If the control signal is logic low (0) then the counter counts in the decreasing order that is down counter. When the control signal is logic high (1) then the counter counts in the increasing order that is up counter.

PROCEDURE :

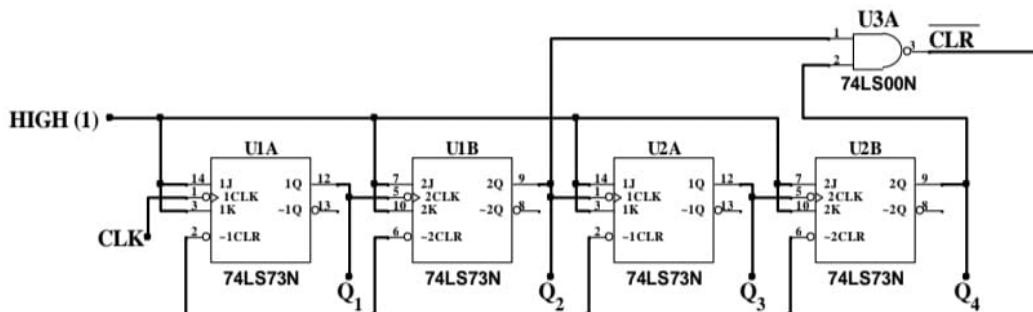
1. Connections are given as per the logic diagram.
2. Apply the clock pulse and verify the truth table.

RESULT :

LOGIC DIAGRAM FOR MOD - 10 RIPPLE COUNTER:



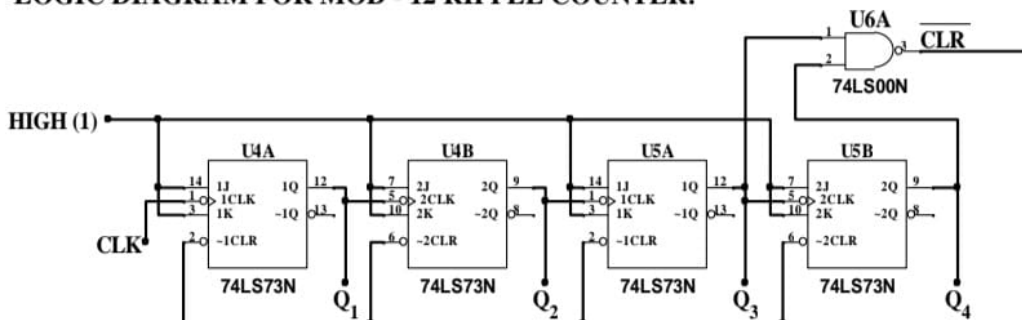LOGIC DIAGRAM FOR MOD - 12 RIPPLE COUNTER:



TRUTH TABLE of MOD-10:

Input CLK	OUTPUTS			
	Q ₄	Q ₃	Q ₂	Q ₁
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	0	0	0	0

TRUTH TABLE of MOD-12:

Input CLK	OUTPUTS			
	Q ₄	Q ₃	Q ₂	Q ₁
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	0	0	0	0

Aim(s) / Objective(s) / Purpose

Answer in a sentence or two, "what is the purpose of this experiment?"

1. Design a 4-bit ripple/asynchronous counter and a mod-10 ripple counter

Introduction / Background

Introduction provides explanation of the topic of experiment. This section should explain the theoretical principles. This section should include block diagrams / logic diagrams where needed. Label the main components, input and output variables. Write equations using an equation writer in a word processor. Draw the truth table / function table / state table where needed.

Tips: Any information copied directly or verbatim from Lab manuals or other references should be stated within quotes and referred, otherwise, it is considered plagiarism

Counter:


A counter is a special type of register which counts a desired sequence of numbers. The main memory element used in implementing counter is FLIP-FLOP. Counters are broadly classified into two types:

- ✧ Asynchronous/Ripple counters
- ✧ Synchronous counters

In this lab we'll look into Asynchronous/ripple counters.

Asynchronous/Ripple counters:

Asynchronous counter is one of the most common counters used to count numbers. In asynchronous counters, clock pulse is connected to one of the flip-flops and the output of that flip-flop is connected to the clock of the second flip-flop. Basically, output of one flip-flop drives the other flip-flop. Asynchronous counters are easy to design for counting numbers of higher order but it has one major drawback: it is slow. Flip-Flop takes time to generate the result. The output of that flip-flop is connected to the clock input of the next flip-flop. As a result, there will be larger delay to generate the output.

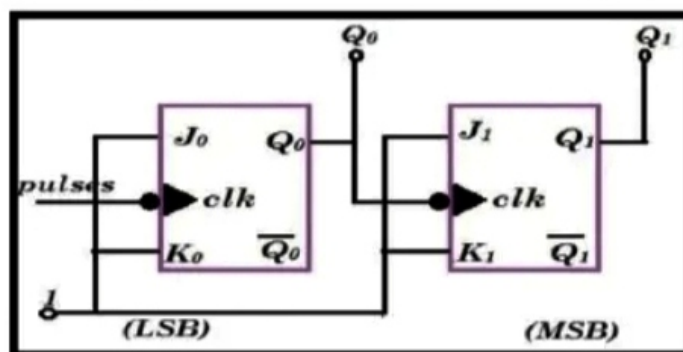

BIT SYNCHRONOUS UP COUNTER

Materials / Equipment

List any and all materials / expendables / equipment / parts you will need for the experiment. Use the proper name and include the number if you need multiples

- ✂ J-K Flip-Flops (×4)
- ✂ AND Gate (IC 7408)
- ✂ Input pins
- ✂ LEDs
- ✂ Clock pulse


Procedure

Write out step by step instructions on how to perform the lab. Include exact measurements if needed. Remember, your goal here is to make this exact experiment reproducible. Be specific. Your procedure should be written so that anyone else could repeat the experiment.

- ✂ Gather all the J-K flip-flops. Connect the first J-K flip-flop to clock pulse. Connect the main output of the first flip flop to the clock input of the second flip-flop. Repeat the same for the rest of the two flip-flops.
- ✂ Connect the inputs of all the J-K flip-flops to active high input because asynchronous counter yields the desired sequence of outputs in TOGGLE state. Connect every output of the J-K Flip-flop to (main output Q) to an LED. The LED connected to the main output of the first J-K Flip-flop (the one connected to the clock pulse) represents the LSB of the output and the LED connected to the last J-K Flip-flop represents the MSB of the output.
- ✂ The counter counts 16 states: 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1101, 1110, 1111.
This is mod-16 ripple counter.
- ✂ For Mod-10 ripple counter, an additional truth table is required to implement the desired output. 4 columns specifying main output of every J-K flip-flop and one column specifying at which state the counter has to reset to the first state (0000 in this case). After the truth table is formed, CLR expression is obtained as a function of output of all the J-K Flip-Flops using K-map. The Boolean expression obtained is implemented with the help of logic gates and is connected to the clear pin of every flip-flop. Hence, the counter starts counting from 0000 and resets after 1001 state. This is MOD-10 ripple counter.


Data

Label clearly what was measured or observed throughout the lab. Include all data tables and/or observation.

 MOD-10 ASYNCHRONOUS COUNTER

TRUTH TABLE FOR MOD-10 ASYNCHRONOUS COUNTER

CLOCK	Q_D	Q_C	Q_B	Q_A	CLEAR
0 (INITIAL)	0	0	0	0	0
↓	0	0	0	1	0
↓	0	0	1	0	0
↓	0	0	1	1	0
↓	0	1	0	0	0
↓	0	1	0	1	0
↓	0	1	1	0	0
↓	0	1	1	1	0
↓	1	0	0	0	0
↓	1	0	0	1	0
↓	1	0	1	0	1
↓	1	0	1	1	X
↓	1	1	0	0	X
↓	1	1	0	1	X
↓	1	1	1	0	X
↓	1	1	1	1	X

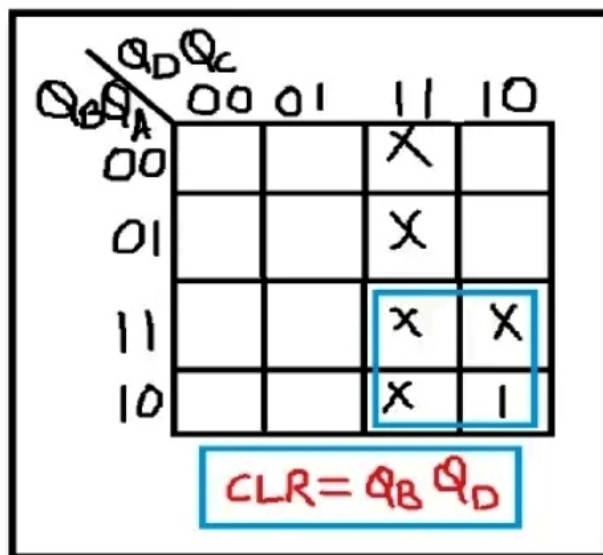

AP FOR CLEAR EXPRESSION

Discussion

If your teacher asks you to answer any discussion (post-lab) questions, this is the place. Write out the questions then answer it below. Be very thorough, detailed and precise. Answer the questions with complete thoughts. Assume the reader does not know anything about this topic.

Results and Conclusion

Summarize your results in the introductory sentence. Relate your results to your objective. Present the results in the easiest way for your reader to understand: graphs, tables, figures, observations, etc., which you make during the lab. All tables and figures should be accompanied by comments or discussions in the text of report; use a numbering system for identification of each one. All figures and tables must have numbers and captions. While the table captions should be placed over the table, figure captions should be placed below the figure.

4-bit asynchronous counter and mod-10 asynchronous counter was implemented successfully.

Experiment No : 11

AIM :

Study shift registers .

APPARATUS REQUIRED :

Sl. No.	COMPONENT	SPECIFICATION	QTY
1.	D FLIP FLOP	IC 7474	2
2.	OR GATE	IC 7432	1
3.	IC TRAINER KIT	-	1
4.	PATCH CORDS	-	35

THEORY :

SHIFT REGISTER :


Shift register is a group of flip- flops that has the capability of storing and shifting the binary information. In digital system the binary datum are re quired to shift in the register from one position to next position. Shift register performs the logic operation shifting of binary data from one flip- flop to next flip- flop. In the shift register, the shifting operation is controlled by common clock pulse. All the flip- flops employed with shift register receives the clock pulse that helps to shift the data from one position to next.

SERIAL-IN-SERIAL-OUT SHIFT REGISTER :

This shift register is constructed in the way of connecting the output of one flip- flop to the input of next flip- flop. All the flip- flops are connected with a common clock pulse. The binary inputs are applied in the input terminal of first flip- flop in series and the outputs are obtained from the output terminal of last flip- flop in series.

TRUTH TABLE OF SERIAL-IN-PARALLEL-OUT SHIFT REGISTER

Clock Pulse	Serial Input	Parallel Output			
	Data In	Q ₁	Q ₂	Q ₃	Q ₄
Initial Vaue	1011	0	0	0	0
After 1 st Clk	1 1 1	1	0	0	0
After 2 nd Clk	11	1	1	0	0
After 3 rd Clk	1	0	1	1	0
After 4 th Clk	-	1	0	1	1

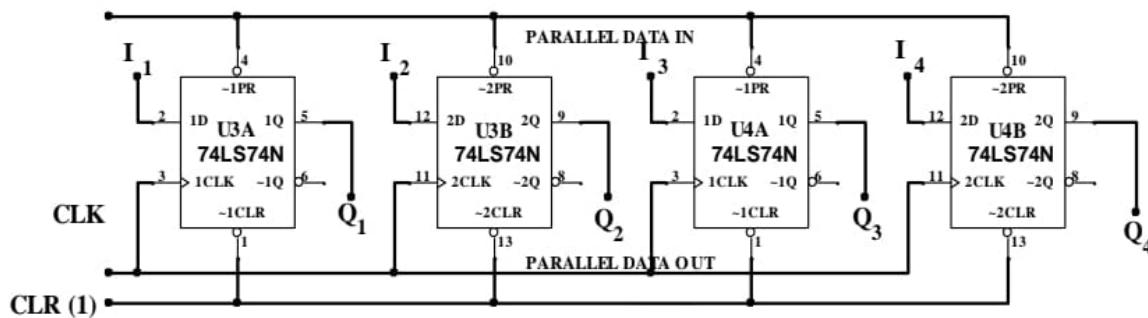LOGIC DIAGRAM: PARALLEL-IN-PARALLEL-OUT SHIFT REGISTER**TRUTH TABLE OF PARALLEL-IN-PARALLEL-OUT SHIFT REGISTER**

Clock Pulse	Parallel Input				Parallel Output			
	I ₁	I ₂	I ₃	I ₄	Q ₁	Q ₂	Q ₃	Q ₄
Initial Value	0	0	0	0	0	0	0	0
After 1 st Clk	1	0	0	0	1	0	0	0
After 2 nd Clk	1	1	0	0	1	1	0	0
After 3 rd Clk	0	1	1	0	0	1	1	0
After 4 th Clk	1	0	1	1	1	0	1	1

SERIAL-IN-SERIAL-OUT SHIFT REGISTER :


This register accepts the binary data in series to provide the output in parallel. In logic diagram the flip- flops are connected similar to SISO shift register that logic diagram is constructed in the way of connecting the output of one flip- flop to the input of next flip- flop. The binary inputs are applied in the input terminal of first flip- flop in series and the outputs are obtained in parallel from the output terminal of each flip- flop employed with register. Hence this configuration is called serial -in-serial-out shift register.

PARALLEL-IN-PARALLEL-OUT SHIFT REGISTER :

This register accepts the binary input in parallel to provide the output in parallel. All the flip- flops present in the register are triggered with common clock pulse. The binary inputs are applied in parallel to all the flip- flops and the outputs are obtained in parallel from the output terminal of each flip- flop employed with register. Hence this configuration is called parallel -in-parallel-out shift register.

PARALLEL-IN-SERIAL-OUT SHIFT REGISTER :

This register accepts the binary input in parallel to provide the output in series from right most flip- flop. The logic diagram is constructed by flip- flop and combination of logic gates. The combinational logic gates are functioning as a control circuit to load the input of shift the stored binary information. A control signal 'shift' is an active high signal i.e., when the control signal line is activated with logic high input a shift register performs the shifting operation. A control signal "Write" is an active low signal i.e., when the control signal line is activated with logic low input a shift register loads the newly appeared input signals into the flip- flops parallel. These logic operations are controlled by the combinational circuits.

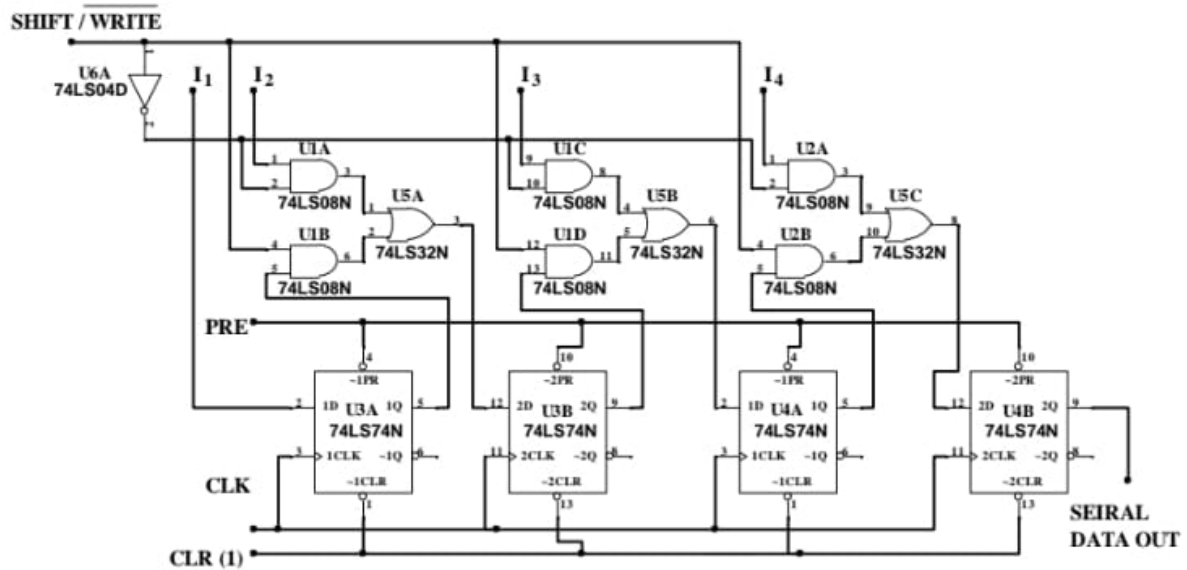LOGIC DIAGRAM: PARALLEL-IN-SERIAL-OUT SHIFT REGISTER**TRUTH TABLE OF PARALLEL-IN-PARALLEL-OUT SHIFT REGISTER**

Control signals		Parallel Input				Serial Output
Clock Pulse	SHIFT / WRITE	I ₁	I ₂	I ₃	I ₄	Q ₄
0	X	0	0	0	0	No Change (Initial state)
1	0	0	0	0	1	1
1	0	1	1	0	0	0
1	1	1	1	0		0
1	1	1	1			0
1	1	1				1
1	1	-				1

PROCEDURE:

- (i) Connections are given as per circuit diagram.
- (ii) Logical inputs are given as per circuit diagram.
- (iii) Observe the output and verify the truth table.

RESULT:

Experiment No : 12

AIM :

Objective: Find 1's & 2's complement of a 8 bit number

Apparatus required: 8085 Simulator, PC.

Program:

1's complement of 8 bit number

LDA 2200H	Get the number
CMA	Complement number
STA 2300H	Store the result
HLT	Terminate program execution

2's complement of a no

LDA 2200 H	Get the number
CMA	Complement the number
ADI 01H	; Add one in the number
STA 2300H	Store the result
HLT	Terminate program execution

Result: 1's & 2's complement of a 8 bit number is executed.

Experiment No : 13(A)

Objective : Addition of two 8-bit numbers.

Apparatus Required: 8085 Simulator, PC.

Program:

MVI C 00	Initialize C register to 00
LDA 4150	Load the value to Accumulator.
MOV B A	Move the content of Accumulator to B register.
LDA 4151	Load the value to Accumulator.
ADD B	Add the value of register B to Accumulator.
JNC LOOP	Jump on no carry.
INR C	Increment value of register C.
LOOP: STA 4152	Store the value of Accumulator.
MOV A C	Move content of Register C to Accumulator
STA 4153	Store the value of Accumulator
HLT	

Obsevation:

Input:	80 (4150)
	80 (4251)
Output:	00 (4252)
	01 (4253)

Result: Thus the program to add two 8 bit numbers was executed.

Experiment No : 13(B)

Objective: Subtraction of two 8-bit numbers.

Apparatus required: 8085 Simulator, PC.

Program:

MVI C 00	Initialize C register to 00
LDA 4150	Load the value to Accumulator.
MOV B A	Move the content of Accumulator to B register.
LDA 4151	Load the value to Accumulator.
SUB B	Add the value of register B to Accumulator.
JNC LOOP	Jump on no carry.
CMA	Complement Accumulator Content
INR A	Increment value of register C.
INR C	Increment value of register C.
LOOP: STA 4152	Store the value of Accumulator.
MOV A C	Move content of Register C to Accumulator
STA 4153	Store the value of Accumulator
HLT	

Observation:

Input:	06 (4150)
	02 (4251)
Output:	04 (4252)
	01 (4253)

Result: Thus the program to subtract two 8 bit numbers was executed.

Experiment No : 14

Objective: Find largest Number From an array.

Apparatus required: 8085 Simulator, PC.

Program:

	LXI	H, 4200	Set pointer for array
	MOV	B, M	Load the count
	INX	H	
	MOV	A, M	Set 1 st element as largest data
	DCR	B	Decrement the count
LOOP:	INX	H	
	CMP	M	If A reg.>M go to AHEAD
	JNC	AHEAD	
	MOV	A, M	Set the new value as largest
AHEAD:	DCR	B	
	JNC	LOOP	Repeat comparisons till count=0
	STA	4300	Store the largest value at 4300
	HLT		

Observation:

Input	05 (4200).....Array size
	0A (4201)
	F1 (4202)
	1F (4203)
	26 (4204)
	FE (4205)

Output	FE (4300)
--------	-----------

Result: Thus the program to find largest number in an array was executed.

Experiment No : 15

Objective: Transfer Block of data bytes from one memory location to another .

Apparatus required: 8085 Simulator, PC.

Program:

	MVI C, 0AH	Initialize counter
	LXI H, 2200H	Initialize source memory pointer
	LXI D, 2300H	Initialize destination memory pointer
BACK	MOV A, M	Get byte from source memory block
	STAX D	Store byte in the destination memory block
	INX H	Increment source memory pointer
	INX D	Increment destination memory pointer
	DCR C	Decrement counter
	JNZ BACK	If counter 0 repeat
	HLT	Terminate program execution

Result: Transfer Block of data bytes from one memory location to another is executed.

Experiment No :- 16 B)1**AIM:**

Traffic Light Controller using 8255

INTRODUCTION

In this modern life, the number of vehicles increase more day by day. The increase of vehicle may cause accidents and other problems on the road. Controlling traffic at regular intervals of time with accuracy and uniformity has become a necessity to avoid accidents, discomfort of drivers. The microprocessor controls the traffic signals very effectively and with accurate timings.

CIRCUIT DESCRIPTION

In this Traffic Light Module one square is shown which has four ends called East, West, North & South. The Traffic Light Module is interfaced with Port A and Port C of 8255. Port A is connected with North and South LEDs. Port C is connected with East and West LEDs. Each end has four LEDs called STOP, START, GO STRAIGHT & GO LEFT.

PORT-A

NORTH				SOUTH			
PA7	PA6	PA5	PA4	PA3	PA2	PA1	PA0
GO-LEFT	GO-STR	START	STOP	GO-LEFT	GO-STR	START	STOP

PORT-B

EAST				WEST			
PA7	PA6	PA5	PA4	PA3	PA2	PA1	PA0
GO-LEFT	GO-STR	START	STOP	GO-LEFT	GO-STR	START	STOP

HARDWARE INSTALLATION


Connect Traffic Light Controller Module to 8255-I of 8051/8085/8086 Trainer kit through 26 pin FRC Cable.

Be sure about the direction of the cable i.e. Pin No. 1 of Module should be connected to Pin No. 1 of 8255 connector.

Connect +5V, GND from the Trainer kit (+5V & GND signals are available in the 25 & 26 pin of FRC 8255-I Connector)

FLOWCHART

3

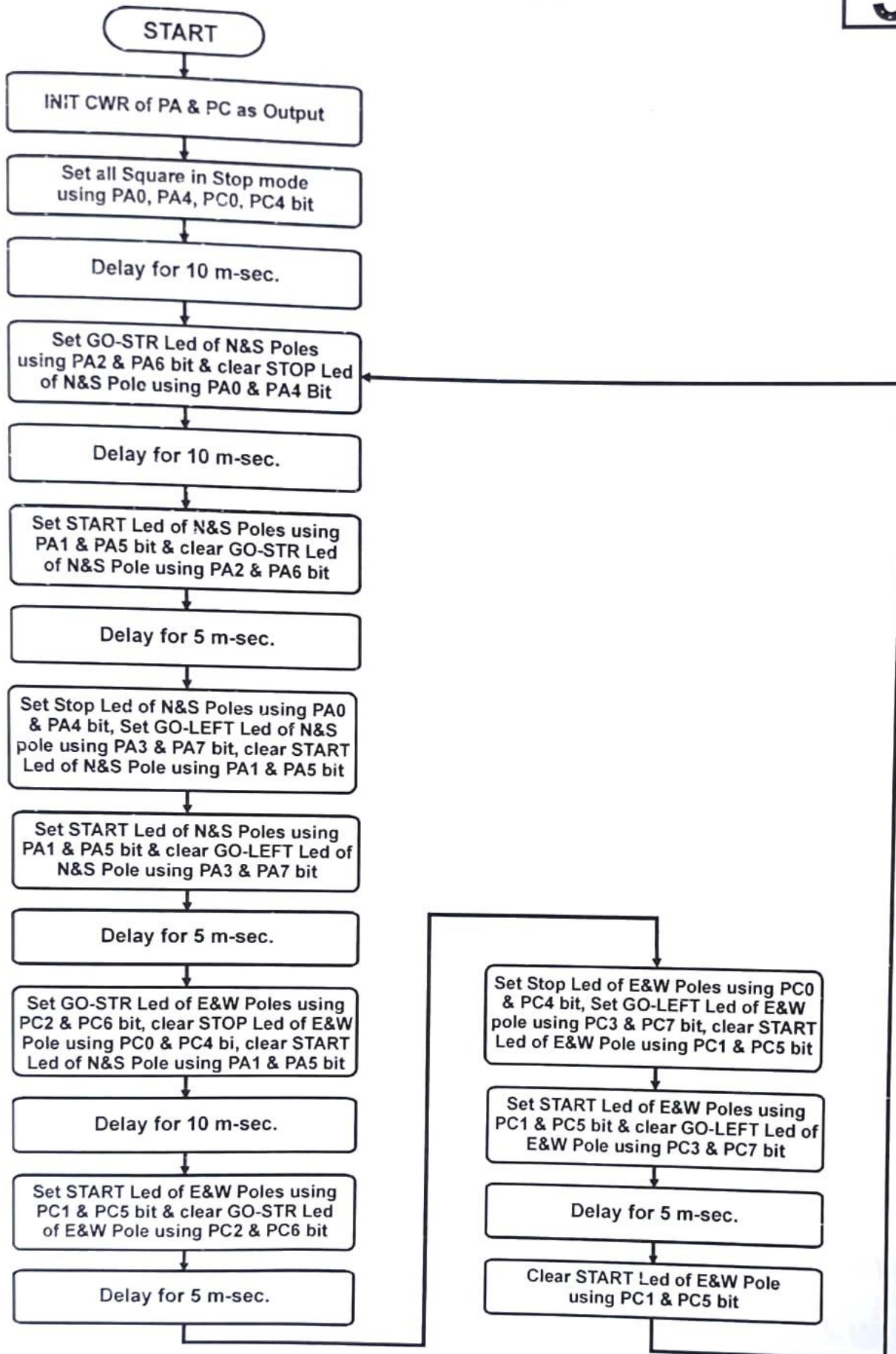

PROGRAMS

4

PROGRAM FOR MICRO-85 LCD TRAINER KIT

8255 Port Address

Port A - 00H
 Port B - 01H
 Port C - 02H
 Control Word - 03H

Program


This program controls Traffic Light of One Square. By changing the delay between Two Signals one can change the Speed of Traffic.

<u>Address</u>	<u>Opcodes</u>	<u>Mnemonics</u>	<u>Comments</u>
2000	3E 80	MVI A,80H	;SET ALL PORTS AS OUTPUT
2002	D3 03	OUT 03H	
2004	3E 11	MVI A,11H	;SET ALL SQUARE RED(STOP)
2006	D3 00	OUT 00H	
2008	D3 02	OUT 02H	
200A	CD 50 20	CALL DELAY1	;CALL DELAY 10MSEC
200D	3E 44	MVI A,44H	;SET GREEN (GO LED) OF N & S
200F	D3 00	OUT 00H	;SET RED (STOP LED) OF E & W
2011	CD 50 20	CALL DELAY1	;CALL DELAY 10MSEC
2014	3E 22	MM A,22H	
2016	D3 00	OUT 00H	;SET YELLOW(START LED) OF N & S
2018	CD 63 20	CALL DELAY2	;CALL DELAY 5 MSEC
201B	3E 99	MVI A,99H	;SET ALL SQUARE RED(STOP)
201D	D3 00	OUT 00H	;SET GREEN(GO-LEFT LED) OF N & S
201F	CD 50 20	CALL DELAY1	;CALL DELAY 10MSEC
2022	3E 22	MM A,22H	
2024	D3 00	OUT 00H	;SET YELLOW(START LED) OF N & S

<u>Address</u>	<u>Opcodes</u>	<u>Mnemonics</u>	<u>Comments</u>
2026	CD 63 20	CALL DELAY2	;CALL DELAY 5 MSEC
2029	3E 11	MM A,11H	;SET ALL SQUARE RED(STOP)
202B	D3 00	OUT 00H	
202D	3E 44	MVI A,44H	;SET GREEN (GO LED) OF E & W
202F	D3 02	OUT 02H	
2031	CD 50 20	CALL DELAY1	;CALL DELAY 10MSEC
2034	3E 22	MVI A,22H	
2036	D3 02	OUT 02H	;SET YELLOW(START LED) OF E & W
2038	CD 63 20	CALL DELAY2	;CALL DELAY 5 MSEC
203B	3E 99	MVI A,99H	;SET ALL SQUARE RED(STOP)
203D	D3 02	OUT 02H	;SET GREEN(GO-LEFT LED) OF E & W
203F	CD 50 20	CALL DELAY1	;CALL DELAY 10MSEC
2042	3E 22	MVI A,22H	;SET YELLOW(START LED) OF E & W
2044	D3 02	OUT 02H	
2046	CD 63 20	CALL DELAY2	;CALL DELAY 5 MSEC
2049	3E 11	MVI A,11H	;SET ALL SQUARE RED (STOP)
204B	D3 02	OUT 02H	
204D	C3 0D 20	JMP LOOP	;JUMP TO LOOP
2050	06 25	DELAY1: MVI B,25H	;10 MSEC DELAY ROUTINE
2052	0E FF	LP3: MVI C,0FFH	
2054	16 FF	LP2: MVI D,0FFH	
2056	15	LP1: DCR D	
2057	C2 56 20	JNZ LP1	
205A	0D	DCR C	
205B	C2 54 20	JNZ LP2	
205E	05	DCR B	
205F	C2 52 20	JNZ LP3	
2062	C9	RET	

<u>Address</u>	<u>Opcodes</u>		<u>Mnemonics</u>		<u>Comments</u>
2063	06 05	DELAY2:	MM	B,05H	;5 MSEC DELAY ROUTINE
2065	0E FF	LP6:	MM	C,0FFH	
2067	16 FF	LP5:	MM	D,0FFH	
2069	15	LP4:	DCR	D	
206A	C2 69 20		JNZ	LP4	
206D	0D		DCR	C	
206E	C2 67 20		JNZ	LP5	
2071	05		DCR	B	
2072	C2 65 20		JNZ	LP6	
2075	C9		RET		

BLOCK DIAGRAM

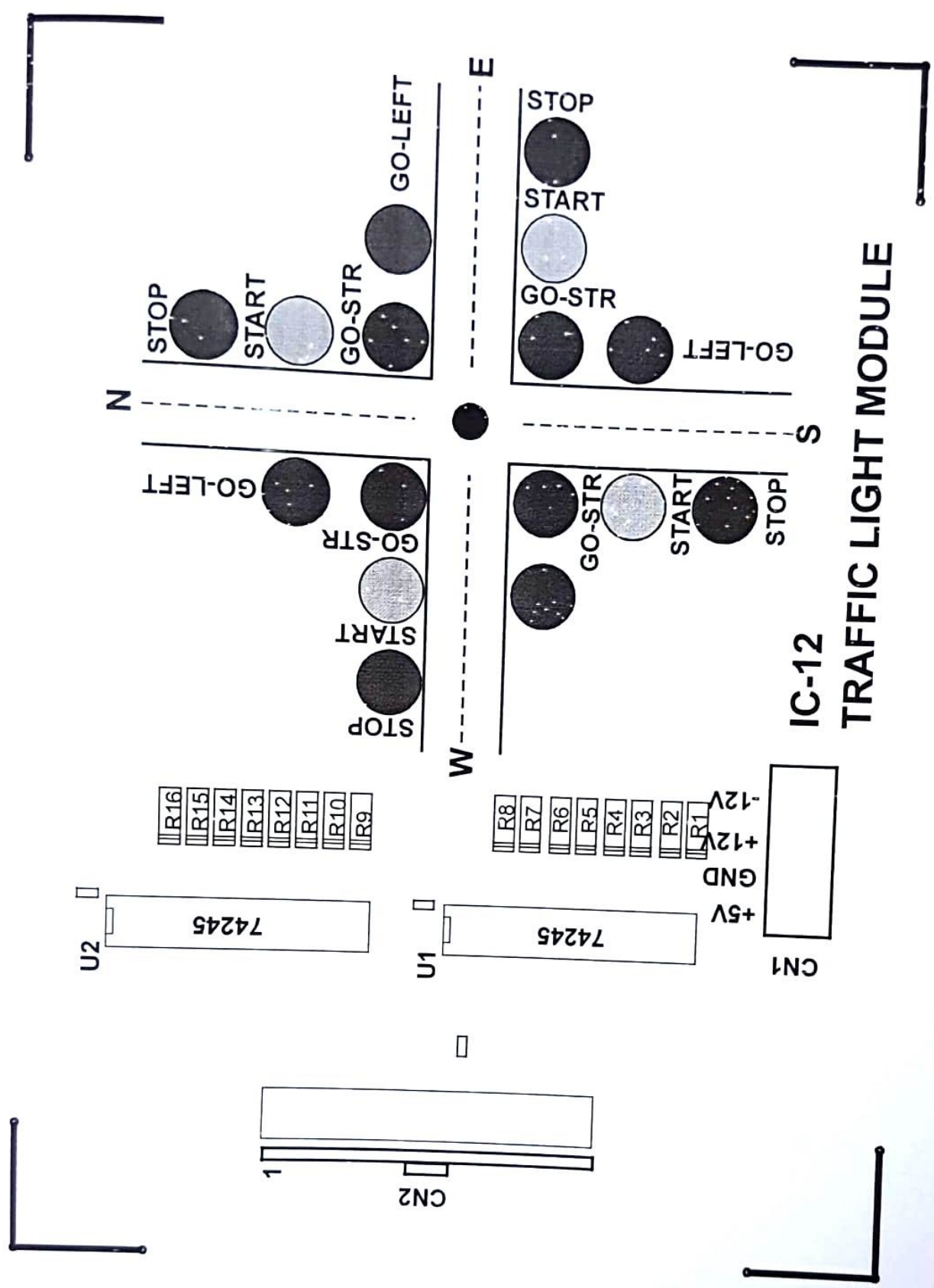

IC-12
TRAFFIC LIGHT MODULE

Experiment No : 16 B 2

AIM

To write a program to generate square wave and triangular wave using microprocessor 8085 by interfacing with a programmable peripheral interface 8255.

THEORY

The Intel 8255 Programmable Peripheral Interface (PPI) chip is a peripheral chip made in DIP 40 and PLCC 44 pins encapsulated versions. The 8255 has 24 input/output pins in all. These are divided into three 8-bit ports. Port A and port B can be used as 8-bit input/output ports. Port C can be used as an 8-bit input/output port or as two 4-bit input/output ports or to produce handshake signals for ports A and B.

The three ports are further grouped as follows:

1. Group A consisting of port A and upper part of port C.
2. Group B consisting of port B and lower part of port C.

Eight data lines (D0 - D7) are available (with an 8-bit data buffer) to read/write data into the ports or control register under the status of the RD (pin 5) and WR (pin 36), which are active low signals for read and write operations respectively. The address lines A_1 and A_0 allow to successively access any one of the ports or the control register as listed below:



The control signal CS (pin 6) is used to enable the 8255 chip. It is an active low signal, i.e., when CS = '0', the 8255 is enabled. The RESET input (pin 35) is connected to the RESET line of system like 8085, 8086, etc., so that when the system is reset, all the ports are initialized as input lines. This is done to prevent 8255 and/or any peripheral connected to it, from being destroyed due to mismatch of ports. As an example, consider an input device connected to 8255 at port A. If from the previous operation, port A is initialized as an output port and if 8255 is not reset before using the current configuration, then there is a possibility of damage of either the input device connected or 8255 or both since both 8255 and the device connected will be sending out data.

The control register or the control logic or the command word register is an 8-bit register used to select the modes of operation and input/output designation of the ports.

ALGORITHM


1. Load the control word into the control register
2. Load the initial value to accumulator and move it to output port.
3. Call the delay program.
4. Load the final value to accumulator and move it to output port.
5. Call the delay program.
6. Repeat steps 2 to 5

FLOW CHART

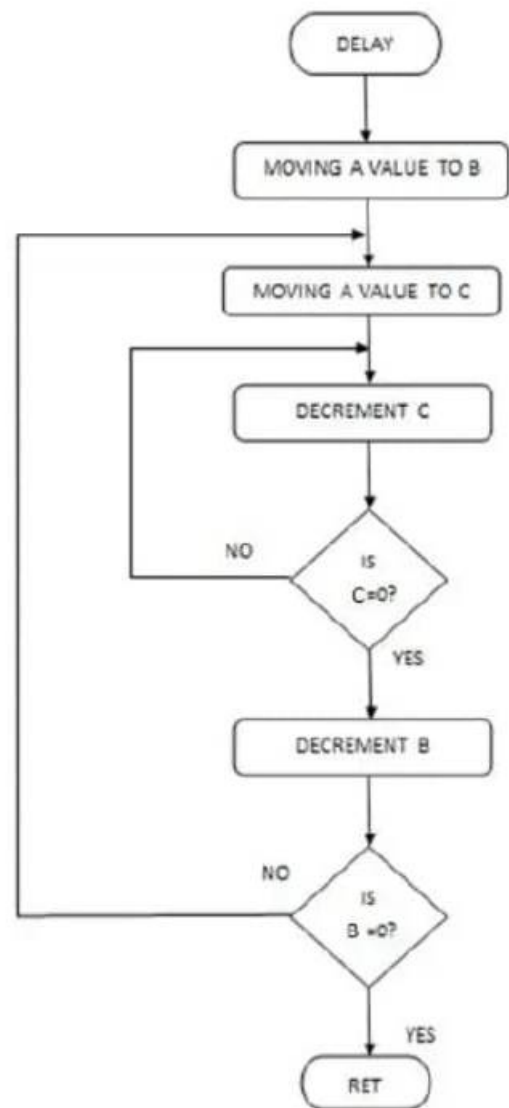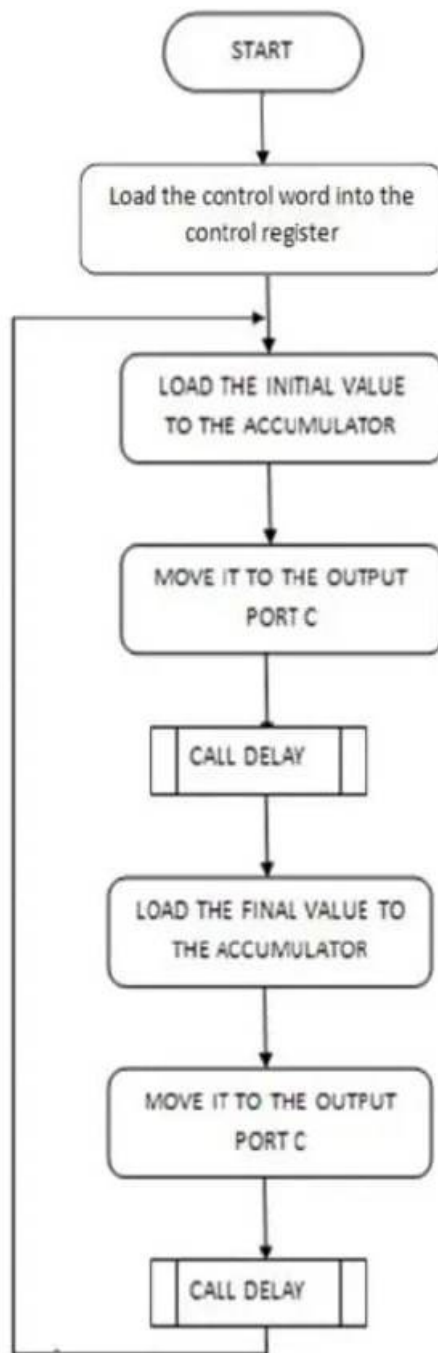

CODING FOR SQUARE WAVE GENERATION


Address	Op Code	Label	Instructions	COMMENTS
4100	3E, 80		MVI A,80	;Control word is initialized
4102	D3, 0F		OUT 0F	;Control register
4104	3E, FF	L	MVI A, 00	; load the initial value to the accumulator
4106	D3,0C		OUT 0C	;output port C
4108	CD,		CALL DELAY	;Call the delay program
410B	3E, 00		MVI A, FF	; load the final value to the accumulator
410D	D3,0C		OUT 0C	; output port C
410F	CD,		CALL DELAY	; Call the delay program
4112	C3		JMP L	;Jump
4115	06	DELAY	MVI B, 05	;move a value to B
4117	0E	L1	MVI C, FF	;move a value to C
4119	0D	L2	DCR C	;decrement the value in C register
411A	C2		JNZ L2	;jump if no zero to loop 2
411D	05		DCR B	;decrement the value in B register
411E	C2		JNZ L1	;jump if no zero to loop 1
4121	C9		RET	;return

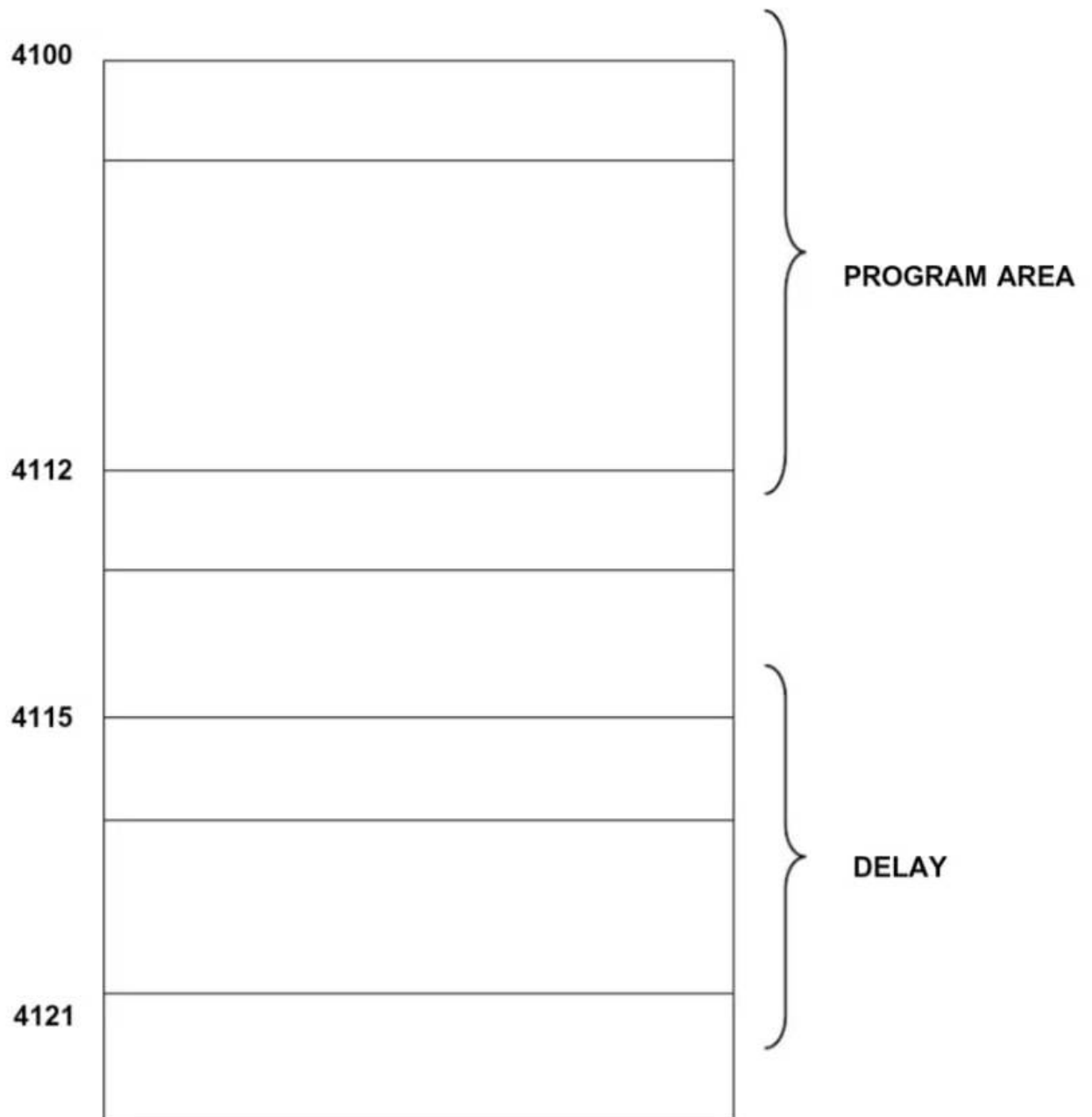MEMORY MAP FOR SQUARE WAVE GENERATION

ALGORITHM


- 1) Load the control word into the control register
- 2) Move 00 into A register
- 3) Move the value of accumulator to port A
- 4) Increment the value in A register by 1.
- 5) If there is no carry repeat from step 3 or else continue with the next step
- 6) Move FF into A register.
- 7) Move the value of accumulator to port A
- 8) Decrement the value at A register by 1.
- 9) If the value in the A register is not zero then repeat step 8 to step 9 or else continue with the next step.
- 10) Go to step 2

FLOW CHART:

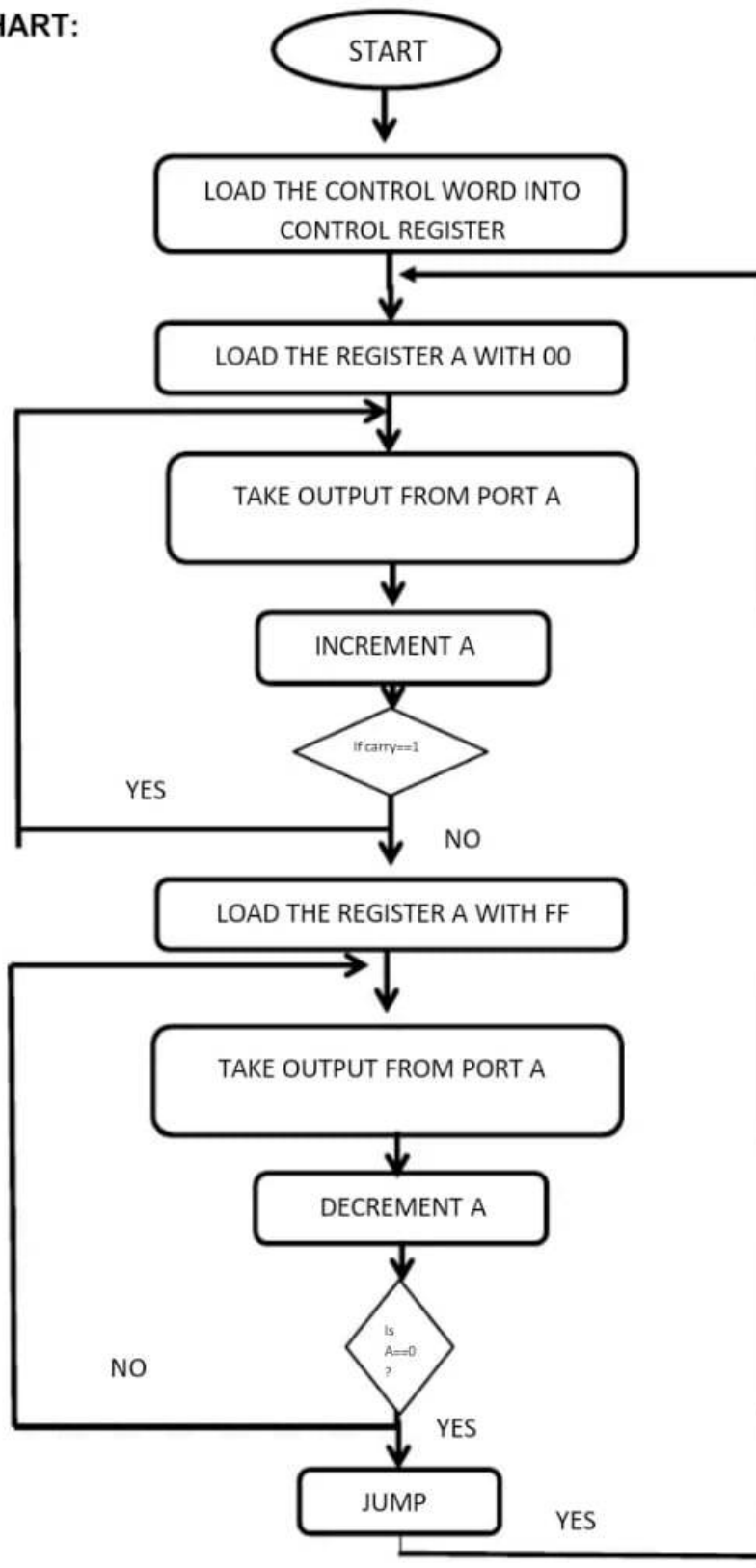

CODING FOR TRIANGULAR WAVE GENERATION

ADDRESS	OPCODE	LABEL	INSTRUCTION	COMMENT
4100	3E,80		MVI A,80	;the value 80 is loaded to accumulator
4103	D3,0F		OUT 0F	;The value in A is loaded into 0F
4105	3E,00	L	MVI A,00	; the value 0 is moved into A register.
4107	D3,0C	L1	OUT A	;the output is taken from port A.
4109	3C		INR A	;the register value A is incremented by 1.
410A	C2,05,41		JC L1	;the zero flag is checked.
410D	3E,FF		MVI A,FF	; the value FF is moved into A register.
410F	D3,0C	L2	OUT A	;the output is taken from port A.
4111	3D		DCR A	;the register value A is decremented by1.
4112	C2,0D,41		JNZ L2	;the zero flag is checked.
4115	C3,00,41		JMP L	;jump to L

 

OUTPUT

When the above code is executed a triangular wave is generated from the output ports of 8255.

RESULT

Thus square wave form and triangular waveform were generated using peripheral programmable device 8255

